

This sequential circuit has its outputs connected to a display with possible outputs from 0 to 7. What sequence of digits will it display as it is clocked? Begin with the state 0 = 000.

